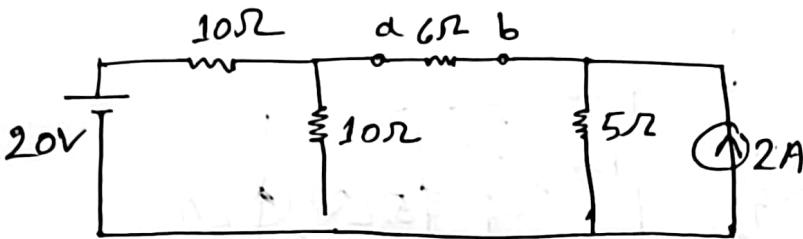


MD. Sohamur Rahman Shimul


Assignment: 03

CSE250 Sec: 02

Q#1



Finding V_{oc} :

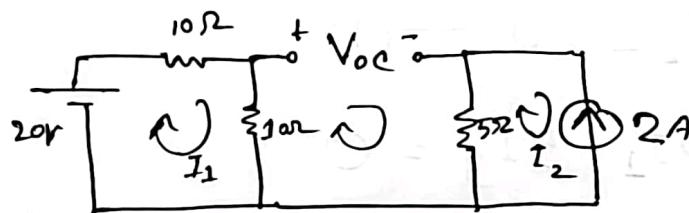

From loop 2:

$$I_2 = -2 \text{ A}$$

From loop 1:

$$10I_1 + 10I_2 = 20$$

$$20I_1 = 20$$


$$\therefore I_1 = 1 \text{ A}$$

$$\begin{aligned}
 V_{oc} &= 5 \times I_2 + 10 \times I_1 \\
 &= 5 \times (-2) + 10 \times 1 \\
 &= 0 \text{ V}
 \end{aligned}$$

$$\therefore V_{th} = V_{oc} = 0 \text{ V}$$

Finding R_{th} :

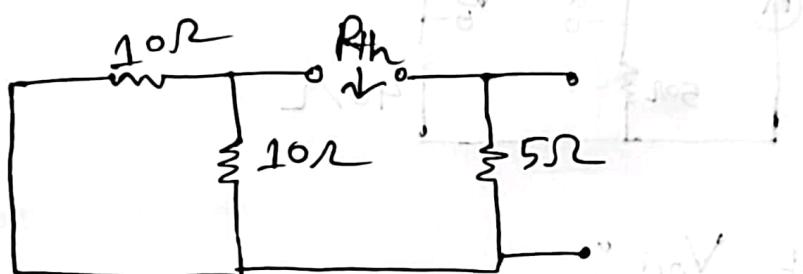
As $V_{th} = 0V$ so kill all the depended source.



$$\therefore R_{th} = \{ (10 || 10) + 5 \} \Omega$$

$$= 10 \Omega$$

Now
Thevenin equivalent circuit:

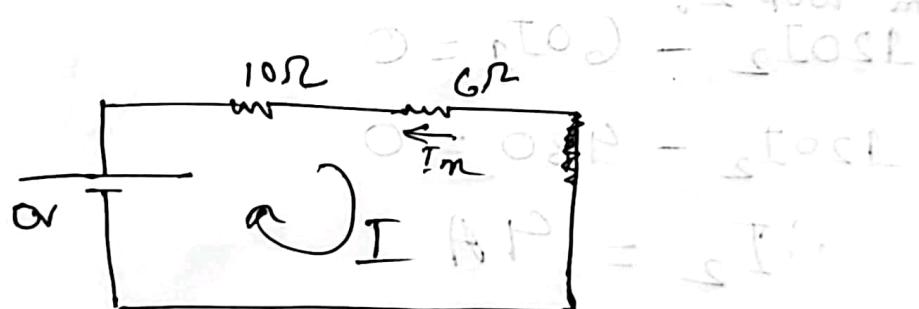


$$1G I = 0_{\text{out}} + s \cos \theta_0 V -$$


$$\therefore I_{\text{in}} = Q A_{\text{in}} = 10s \times 10s$$

and, $I_m = -I = 0A$


(Am)

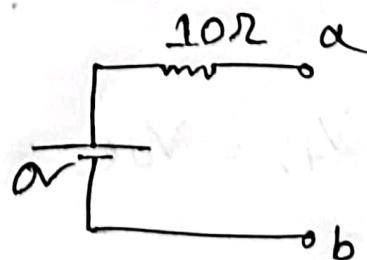

Q#2

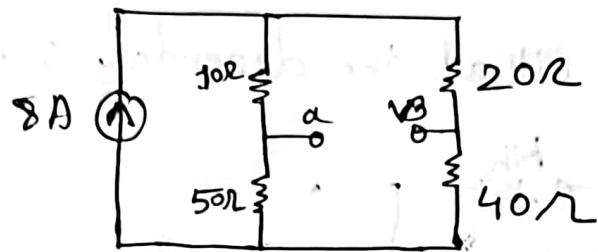

Finding V_{OC} :

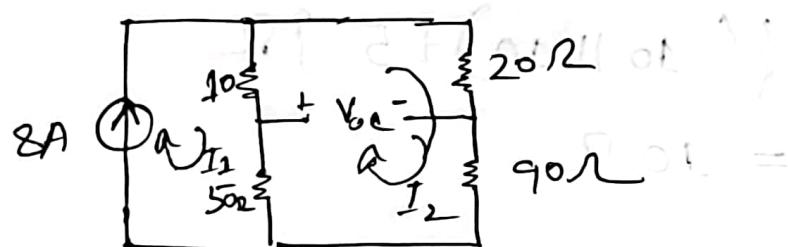

$$\begin{aligned} I_1 &= 8A \\ \text{from loop 2:} \quad 120I_2 - 60I_1 &= 0 \end{aligned}$$

$$120I_2 - 480 = 0$$

$$\therefore I_2 = 4A$$


~~$$-V_{OC} + 20I_2 + 10I_2 - 10I_1 = 0$$~~

~~$$20I_2 - 10I_1 = V_{OC}$$~~

$$\therefore V_{OC} = 40V$$


$$\therefore V_{th} = V_{OC} = 40V$$

finding $E_{scR_{th}}$

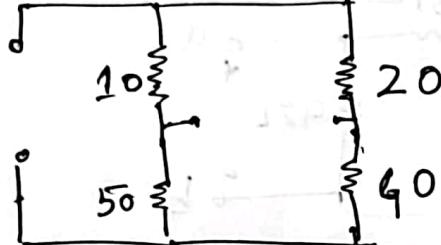

$$R_{eq} = (10+20) \parallel (50+40)$$
$$= 22.5 \Omega$$
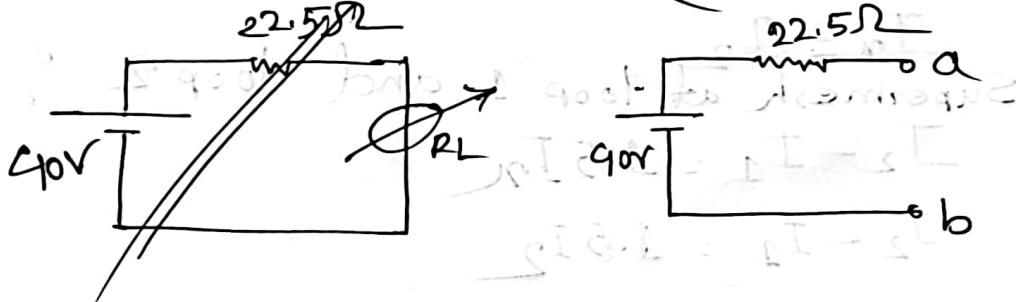
$$\therefore R_{th} = R_{eq} = 22.5 \Omega \quad (\text{Ans})$$



$$I = \frac{40}{22.5} = 1.78 A$$

$$I = 1.78 - 1.78 = 0 A$$

$$I = 1.78 + 1.78 = 3.56 A$$


$$I = 1.78 + 1.78 = 3.56 A$$

① ② are parallel


$$3.56 = 1.78$$

$$A = 1.78$$

Q#3

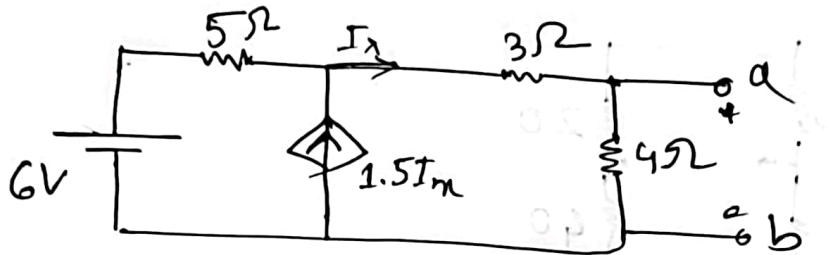

finding V_{OC}

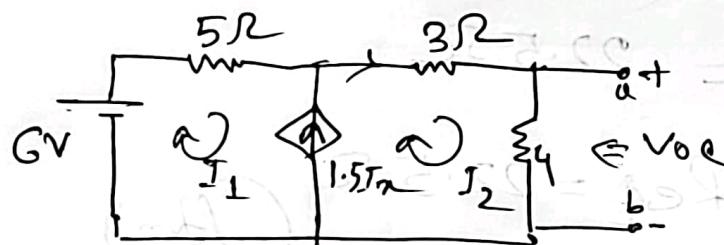

$I_x = I_2$
Supermesh at loop 1 and loop 2.

$$I_2 - I_1 = 1.5I_x$$

$$I_2 - I_1 = 1.5I_2$$

$$I_2 - 1.5I_2 - I_1 = 0$$

$$-I_1 - 0.5I_2 = 0 \quad \text{--- (1)}$$

$$5I_2 + 3I_2 + 4I_2 = 6$$

$$5I_1 + 7I_2 = 6 \quad \text{--- (2)}$$

Solving equ (1), (2)

$$I_1 = -\frac{2}{3} A$$

$$I_2 = \frac{4}{3} A$$


$$V_{OC} = 4I_2$$

$$\therefore = 4 \times \frac{4}{3}$$

$$= 5.33 V$$

$$V_{TH} = V_{OC} = 5.33 V \quad (\text{Ans})$$

finding I_{SC} :

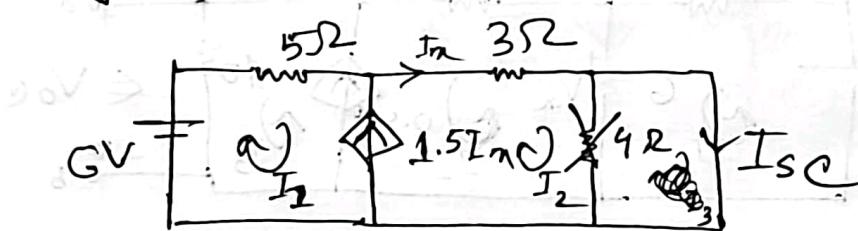

$$I_{SC} = I_2$$

$$I_2 - I_1 = 1.5I_m$$

$$-I_1 - 0.5I_2 = 0 \quad \text{--- (1)}$$

$$5I_1 + 3I_2 - 4I_3 = 6 \quad \text{--- (2)}$$

~~$$-I_1 + 7I_2 = 4I_3$$~~


solving equ (1), (2) \Rightarrow

$$I_1 = -6 A$$


$$I_2 = 12 A$$

$$\therefore R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{5.33}{12} \Omega$$


$$= 0.4467 \Omega \quad (\text{Ans.})$$

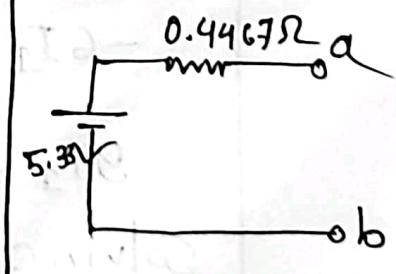

Q#4

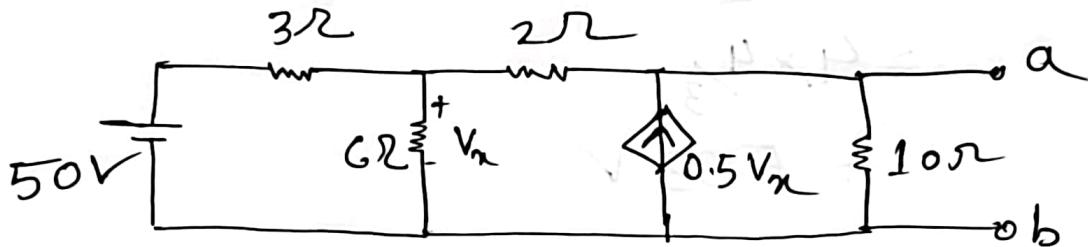

finding V_{OA} :

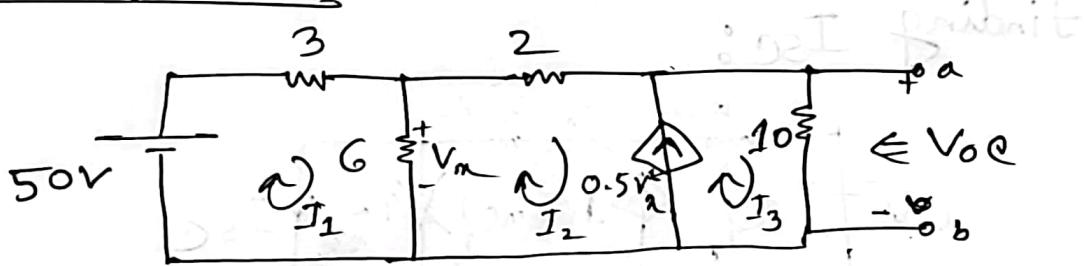

$$I_3 - I_2 = 0.5V_m \quad [V_x = 6(I_1 - I_2)]$$

$$I_3 - I_2 = 3(I_1 - I_2)$$

$$I_3 - I_2 - 3I_1 + 3I_2 = 0$$

$$-3I_1 + 2I_2 + I_3 = 0 \quad \text{--- (1)}$$

$$2I_2 + 10I_3 + 6I_2 - 6I_1 = 0$$

$$-6I_1 + 8I_2 + 10I_3 = 0 \quad \text{--- (2)}$$

$$9I_1 - 6I_2 = 50 \quad \text{--- (3)}$$

Solving (1), (2), (3) \Rightarrow

$$I_1 = -\frac{50}{3} A$$

$$I_2 = -\frac{10}{3} A$$


$$I_3 = \frac{5}{3} A$$

$$V_{OC} = 10I_3$$

$$\Rightarrow 10 \times \frac{50}{3}$$

$$= 166.67 V$$

Finding I_{SC} :

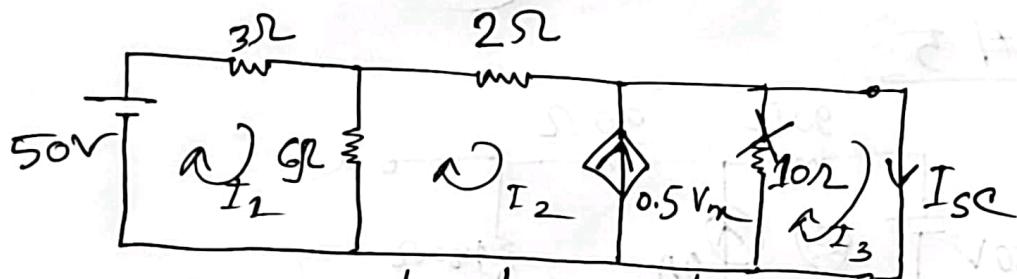

Supermesh at I_2 and I_3 :

$$I_3 - I_2 = 0.5 V_m$$

$$\Rightarrow -3I_1 + 2I_2 + I_3 = 0 \quad \textcircled{I}$$

$$2I_2 + GI_2 - GI_1 = 0$$

$$-GI_1 + 8I_2 = 0 \quad \textcircled{II}$$

From loop 1:

$$9I_1 - GI_2 = 50 \quad \textcircled{III}$$

Solving eqn $\textcircled{I}, \textcircled{II}, \textcircled{III} \Rightarrow$


$$I_1 = 100/9$$

$$I_2 = 25/3$$


$$I_3 = 50/3$$

$$I_{SC} = I_3 = \frac{50}{3} = 16.667 A$$

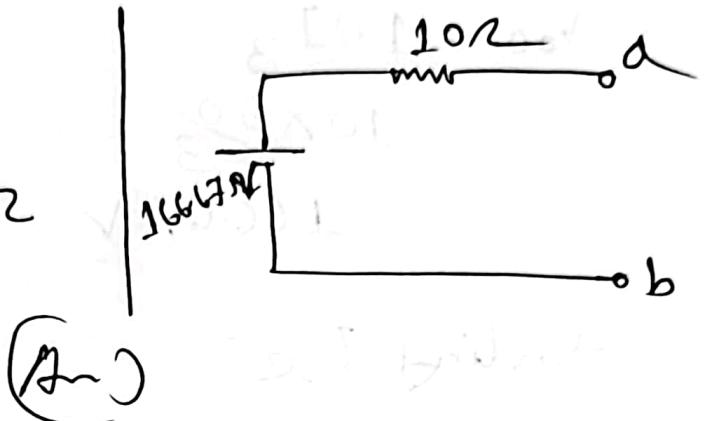
$$\begin{aligned}\therefore R_{th} &= \frac{V_h}{I_{SC}} \\ &= \frac{166.67}{16.67} \Omega \\ &= 10 \Omega\end{aligned}$$



Q# 5

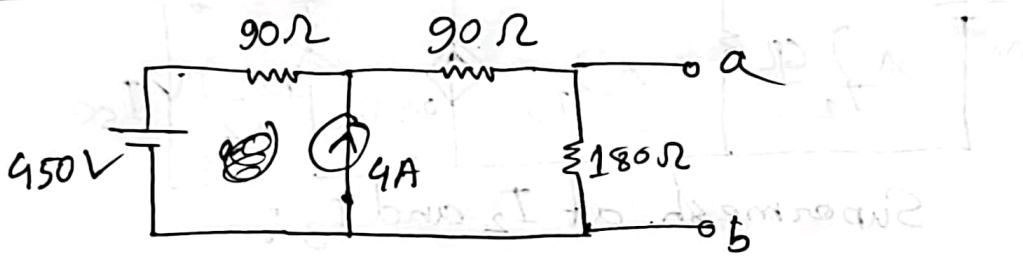

Finding I_{SC}

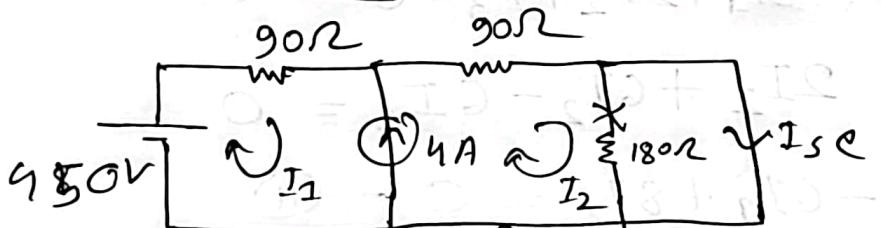

from supermesh ① and ②

$$I_2 - I_1 = 9 \quad \text{--- (1)}$$

and

$$90I_1 + 90I_2 = 950 \quad \text{--- (II)}$$


Solving equ (1) and (II) \Rightarrow

$$I_1 = 0.5 A$$

$$I_2 = 4.5 A$$

$$I_N = I_{SC} = I_2 = 4.5 A \quad (\text{Ans})$$

finding R_N :

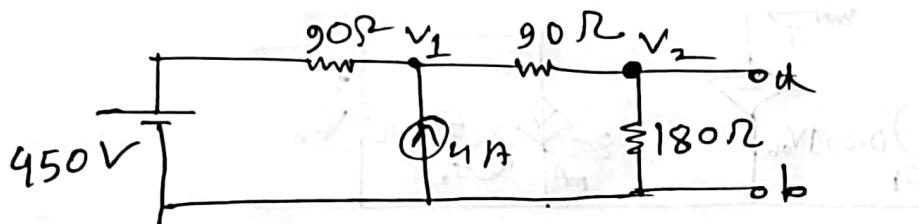

from node 1 \Rightarrow

$$\frac{v_1 - 450}{90} + \frac{v_1 - v_2}{90} - 4 = 0$$

$$\frac{v_1}{90} - 5 + \frac{v_1}{90} - \frac{v_2}{90} - 4 = 0$$

$$v_1 \left(\frac{1}{90} + \frac{1}{90} \right) - v_2 \left(\frac{1}{90} \right) = 9 \quad \text{--- (1)}$$

from node 2 \Rightarrow

$$\frac{v_2 - v_1}{90} + \frac{v_2}{180} = 0$$


$$-\frac{v_1}{90} + v_2 \left(\frac{1}{90} + \frac{1}{180} \right) = 0 \quad \text{--- (2)}$$

Solving eqn (1) and (2) \Rightarrow


$$v_1 = 607.5 V$$

$$v_2 = 40.5 V$$
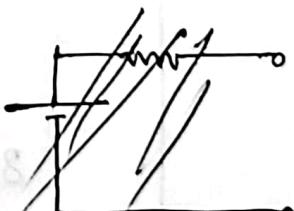
$$\therefore R_N = \frac{v_2}{I_N} = \frac{40.5}{4.5} = 90 \Omega$$




(Ans)

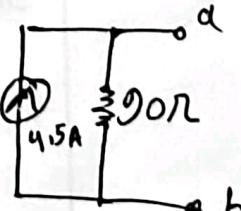


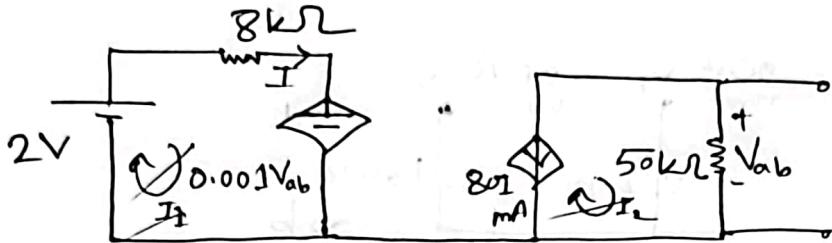Q4G

(as we have option to do (Thevenin / Norton) we will find V_{th} and R_{th})



finding V_{oc} :

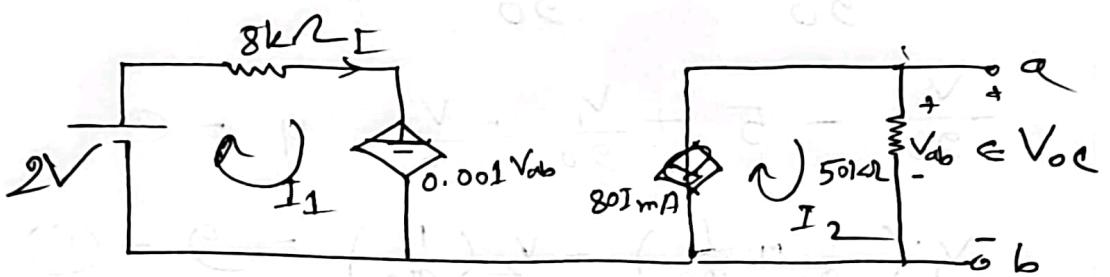

from loop 1

$$8I_1 + 0.001V_{ab} = 2 \quad [V_{ab} = 50I_2]$$

$$8I_1 + 0.001(50I_2) = 2$$

$$8I_1 + 0.05I_2 = 2 \quad \text{--- (1)}$$

from loop 2

$$I_2 = -80I_1 \quad [I = I_1]$$

$$I_2 = -80I_1$$

$$80I_1 + I_2 = 0 \quad \text{--- (2)}$$

Solving equ (1) and (2) \Rightarrow


$$I_1 = 0.5 \text{ mA}$$

$$I_2 = -40 \text{ mA}$$

$$V_{OC} = 50 \times -40 \\ = -2000V$$

$$\therefore V_{TH} = V_{OC} = -2000V$$

Finding R_{TH} I_{SC} :

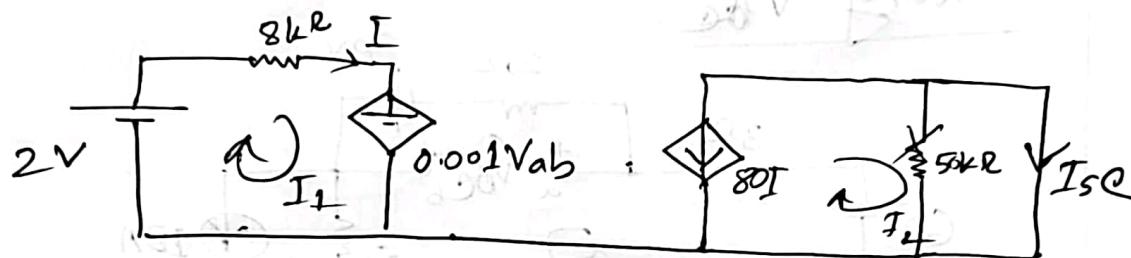

From loop 1:

$$8I_1 + 0.001 V_{ab} = 2 \quad [\because V_{ab} = 0]$$


$$8I_1 = 2$$

$$\therefore I_1 = 0.25 \text{ mA}$$


From loop 2:

$$I_2 = -80I \quad [\because I = I_1 = 0.25 \text{ mA}] \\ = -20 \text{ mA}$$

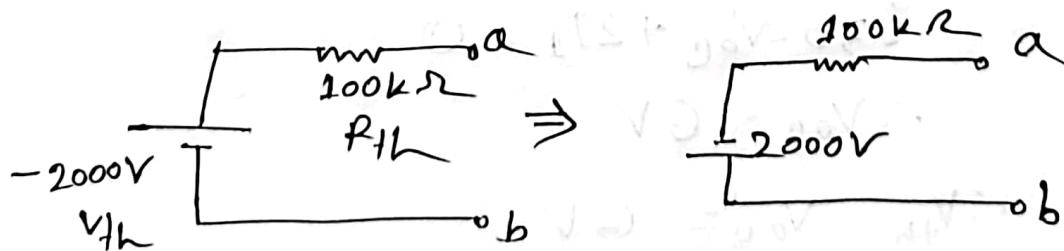
$$\therefore R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{-2000}{-20} = 100 \text{ k}\Omega$$



Q#7

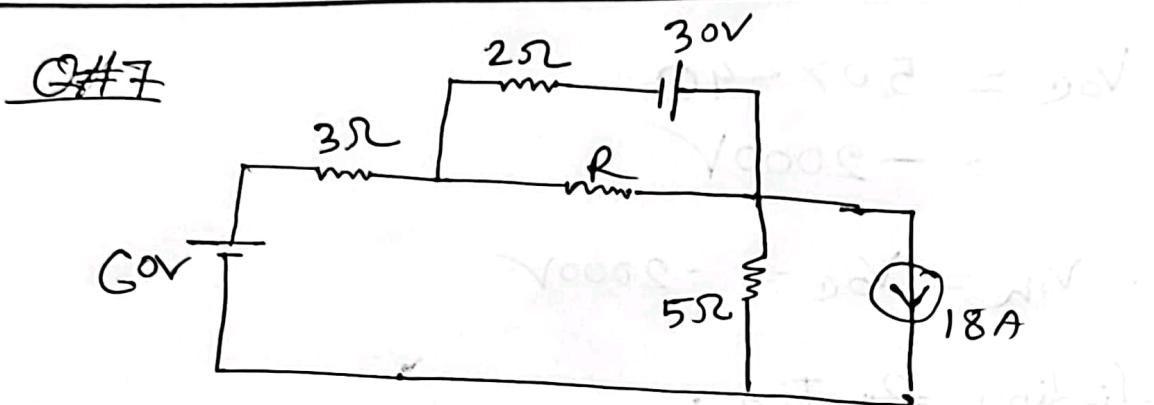

Finding V_{TH} :

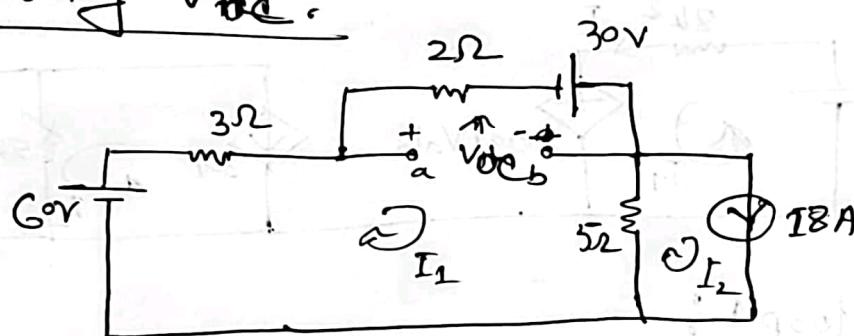

at loop 2

$$+I_2 = 18 \text{ A}$$

at loop 1

$$3I_1 + 2I_2 - 30 + 5I_1 - 5I_2 = 60$$

$$10I_1 - 5I_2 = 90$$

$$\therefore 10I_1 - 5 \times 18 = 90$$

$$\therefore I_1 = 18 \text{ A}$$


Now,

$$-30 - V_{oC} + 2I_1 = 0$$

$$\therefore V_{oC} = GV$$

$$\therefore V_{TH} = V_{oC} = GV$$

Finding I_{SC} :

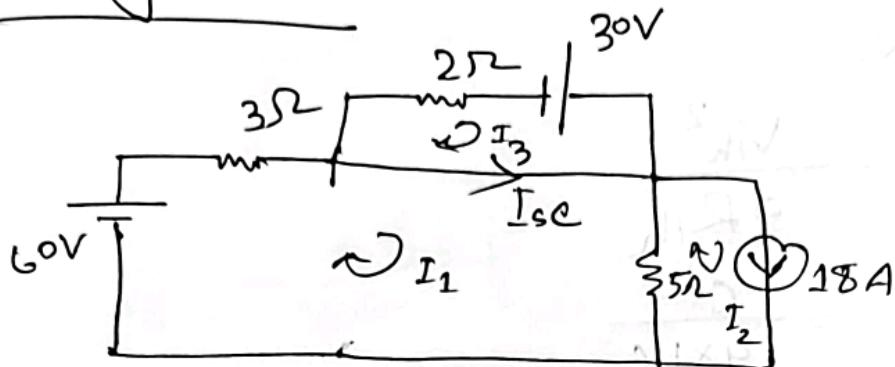

at loop 1

$$8I_1 - 5I_2 = 60 \quad \text{---(1)}$$

at loop 2

$$I_2 = 18 \text{ A}$$

at loop 3

$$2I_3 = 30$$

$$\therefore I_3 = 15 \text{ A}$$

Putting I_2 value at eqn (1)

$$I_1 = 18.75 \text{ A}$$


$$\begin{aligned}\therefore I_{SC} &= I_1 - I_3 \\ &= (18.75 - 15) \text{ A} \\ &= 3.75 \text{ A}\end{aligned}$$

$$\therefore R_{th} = \frac{V_{th}}{I_{SC}} = \frac{6}{3.75} = 1.6 \Omega$$


Now,

We know,

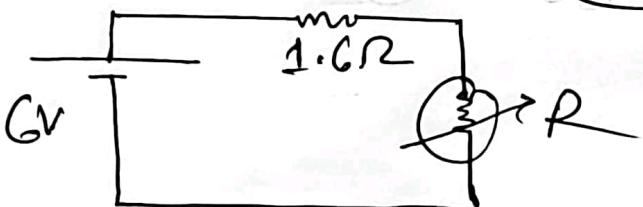
$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$
$$= \frac{G^2}{4 \times 1.6}$$
$$= 5.625 \text{ W}$$



Q48

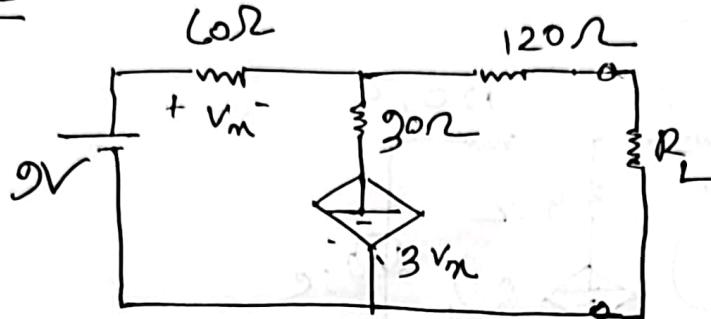

finding V_{cL} :

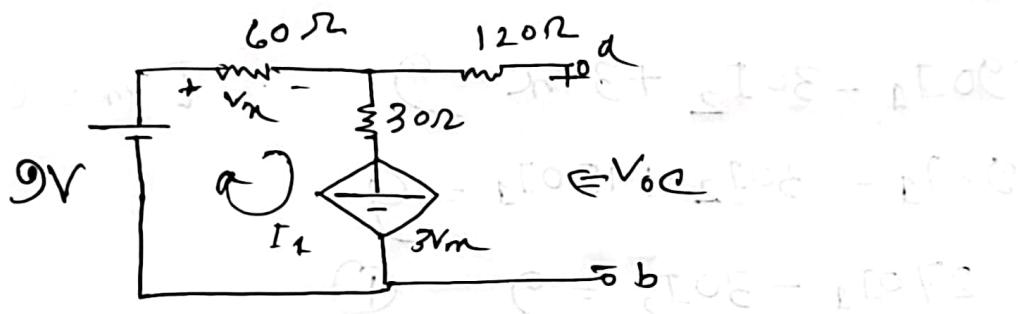

KVL at loop 1:

$$90I_1 + 3V_m = 9$$

$$90I_1 + 3(CoI_1) = 9$$

$$90I_1 + 180I_1 = 9$$

$$\therefore I_1 = \cancel{0.09} A \quad \frac{1}{30} A$$

$$V_{cL} = 3V_m + 30I_1$$


$$V_{cL} = 3(Co \times \cancel{\frac{1}{30}}) + 30 \times \cancel{\frac{1}{30}}$$

$$= \cancel{5.4} + 0.9 = 7V$$

$$= \cancel{7.5V}$$

$$V_{th} = V_{cL} = 7V$$

Finding I_{SC} :

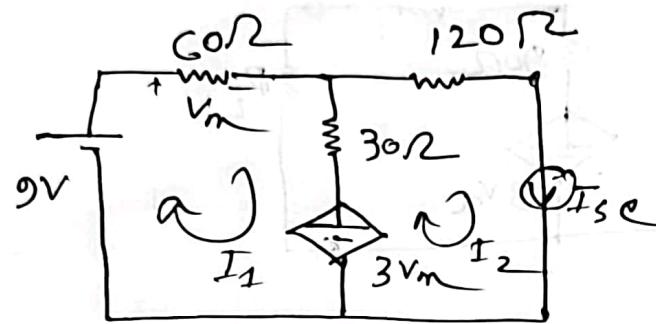

at loop 1

$$90I_1 - 30I_2 + 3V_m = 9 \quad [V_m = 60I_1]$$

~~$$90I_1 - 30I_2 + 180I_1 = 9$$~~

$$270I_1 - 30I_2 = 9 \quad \text{--- (1)}$$

at loop 2

~~$$150I_2 - 30I_1 - 3V_m = 0$$~~

~~$$150I_2 - 30I_1 - 180I_1 = 0$$~~

$$-210I_1 + 150I_2 = 0 \quad \text{--- (II)}$$

Solving eqn (1), (II)

$$I_1 = 0.099A$$

$$I_2 = 0.0552A$$


$$I_{SC} = I_2 = 0.055A$$

$$\therefore R_{th} = \frac{V_{th}}{I_{SC}} = \frac{457}{0.0552} = \cancel{81.27} \cancel{126.81} \Omega$$



$$\begin{aligned} P_{max} &= \frac{V_{th}^2}{4 \times R_{th}} \\ &= 0.0967W \\ &= 96.70mW \end{aligned}$$

(Ans)

Q#9

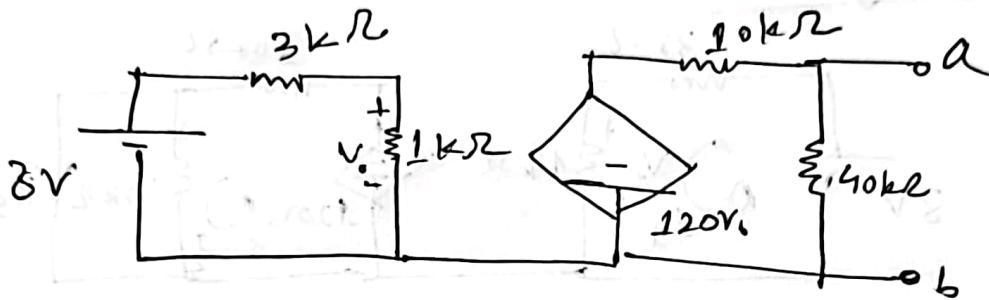

finding V_{OC}

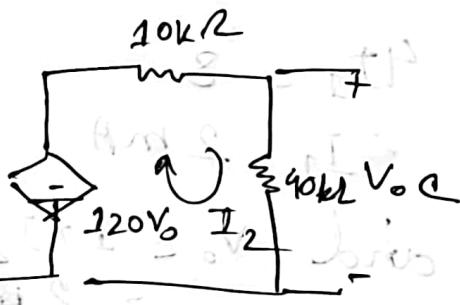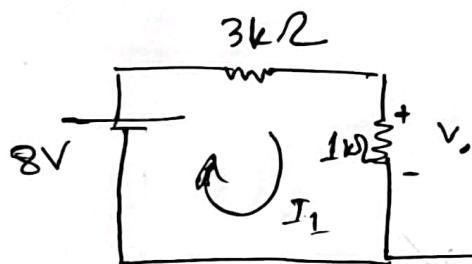

at loop 1

$$3I_1 + 1I_1 = 8$$

$$I_1 = 2 \text{ mA}$$

$$V_o = \frac{1 \times I_1}{1k\Omega} = 2 \text{ V}$$

at loop 2


$$40I_2 + 10I_2 + 120V_o = 0$$

$$40I_2 + 10I_2 = -120 \times 2$$

$$\therefore I_2 = -4.8 \text{ mA}$$

$$\begin{aligned} \therefore V_{OC} &= 40 \times I_2 \\ &= 40 \times (-4.8) = -192 \text{ V} = V_{Th} \end{aligned}$$

finding I_{SC}

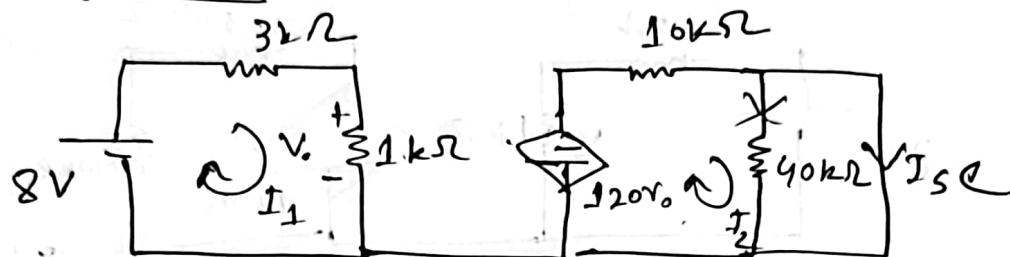

at loop 1

$$4I_1 = 8$$

$$\therefore I_1 = 2 \text{ mA}$$

and $V_o = 1 \times I_2$
 $= 2 \cancel{mA} \checkmark$

at loop 2

$$10I_2 + 120V_o = 0$$

$$10I_2 = -120 \times 2$$

$$\therefore I_2 = -24 \text{ mA}$$

$$\therefore I_{SC} = I_2 = -24 \text{ mA}$$

$$\therefore R_{th} = \frac{V_{th}}{I_{SC}}$$

$$= \frac{-192}{-24}$$


$$= 8 \text{ k}\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$


$$= \frac{(-192)^2}{4 \times (8 \times 10^3)}$$

$$= 1.152 \text{ W (Ans)}$$

Q#10

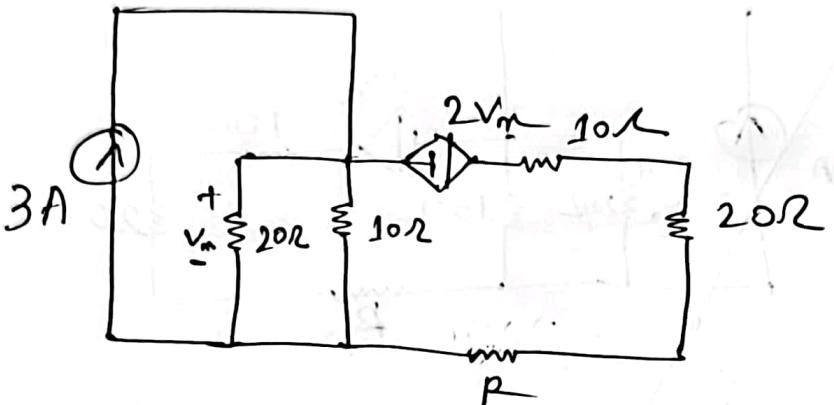

Finding V_{OC}

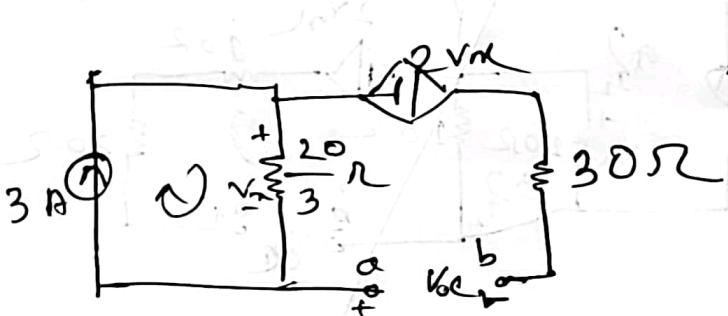

$$I_1 = 3A$$


$$V_m = \frac{20}{3} \times 3 = 20V$$

$$\begin{aligned} V_{OC} &= -2V_m + 30I_1 + \frac{20}{3}I_1 \\ &= -40 + 90 + 20 \end{aligned}$$

$$\begin{aligned} V_{OC} &= -(V_m + 2V_m) + \cancel{+ \frac{20}{3}I_1} \\ &= -(3V_m) \\ &= -3 \times 20 \\ &= -60V \end{aligned}$$

$$\therefore V_{Th} = V_{OC} = -60V$$

Finding R_{th} :

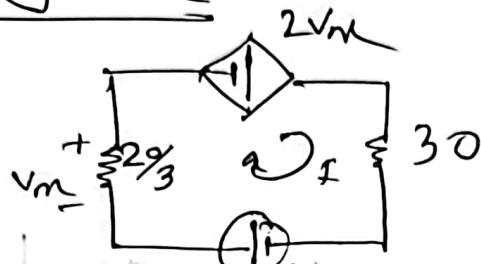

$$\left(\frac{20}{3} + 30\right)I - 2V_m = 1$$
$$\therefore I = \frac{1}{50}$$

$$\therefore R_{th} = \frac{V_m}{I} = \frac{1}{1/50} = 50 \Omega$$

$$So, P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(-50)^2}{4 \times 50}$$
$$= 18 W \quad (\text{Ans})$$